

PART B - Exp - I


Aim:- Study of different theorems for DC and AC circuits.

Apparatus:- DC Source, AC Source, Resistor, Current Source, Voltage source, wire circuit, R.P.S.

Theory:- a) Superposition Theorem b) Thevenin's theorem
c) Norton Theorem d) Max Power transfer theorem


a) Superposition:- statement:- In an linear, bilateral network the response in any element is equal to sum of individual responses while all other sources are non-operative.

Circuit diagram:-

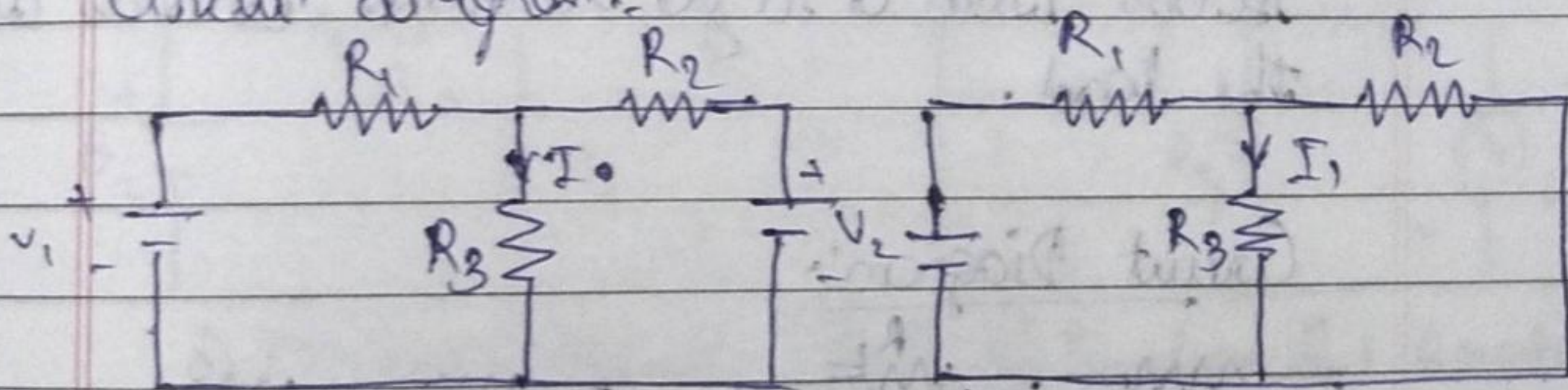

a) Both source are acting (V_1 and V_2)

b) Voltage source V_1 acting alone

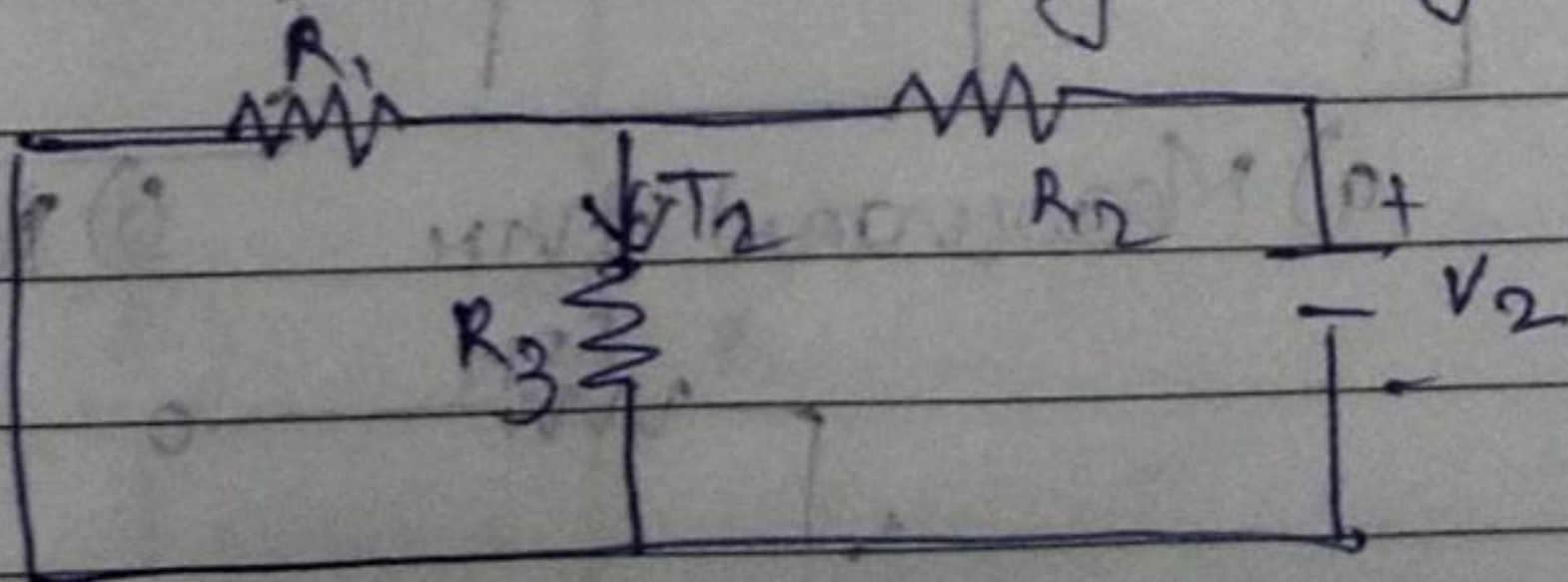

c) Voltage source V_2 acting alone.


- Procedure:-
- 1) Connect the circuit as shown in
 - 2) Find current through R_3 and consider as I_1
 - 3) Connect the circuit as shown in
 - a) note down I_1
 - 3) Connect the circuit as shown in
 - a) note down I_2
 - 4) Verify for $I = I_1 + I_2$

Conclusion:- $I = I_1 + I_2$ i.e. Superposition theorem is verified.

b) Thevenin's Theorem:-


Statement:- Any linear bilateral circuit containing several voltage and resistance can be replaced by just one single voltage in series with a single resistance connected across the load.

Circuit Diagram:-

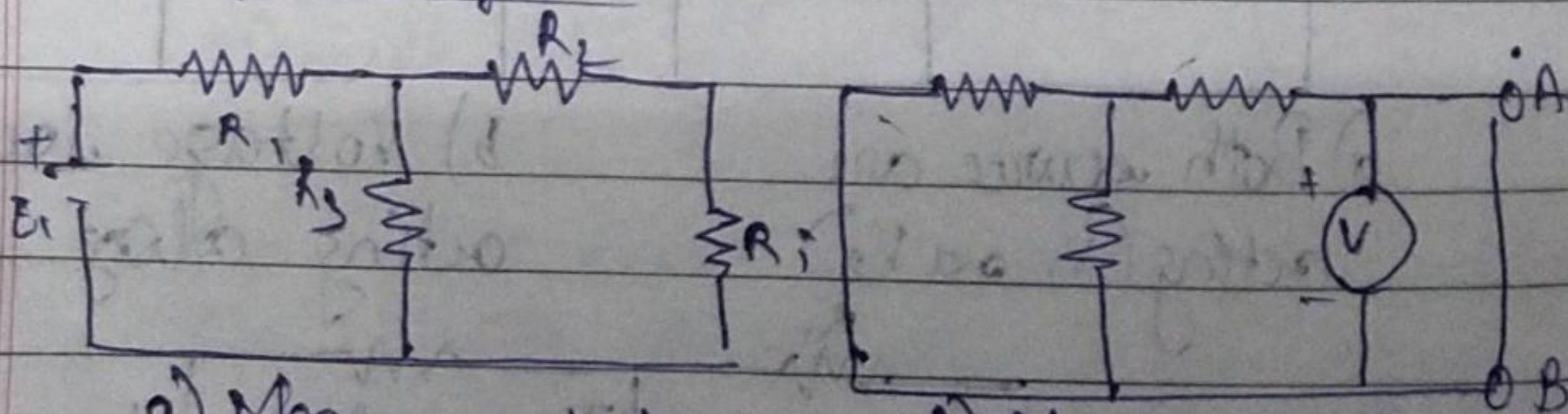

a) Measurement of V_{TH}

b) Measurement of R_{TH}

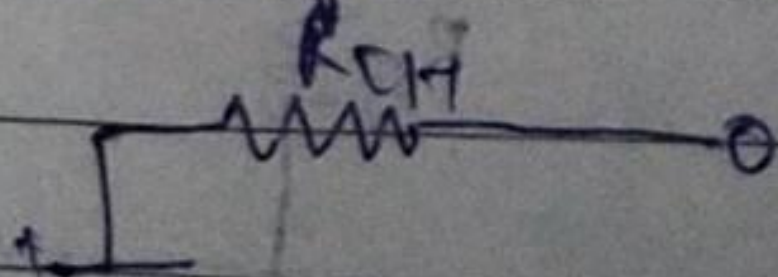

c) Measurement of I_c ($I_c = V_{TH} / R_{TH}$)

Procedure: i) Connect the circuit diagram as shown in (a) Measure V .


ii) Connect the circuit as shown in (b) Measure R_{th} .

iii) Draw the Norton's equivalent circuit as shown in (c). Measure R_L .

c) Norton Theorem:-


Statement:- Any linear bilateral circuit containing several energy sources and resistances can be replaced by a single constant current generator in parallel with a single resistor.

Circuit Diagram

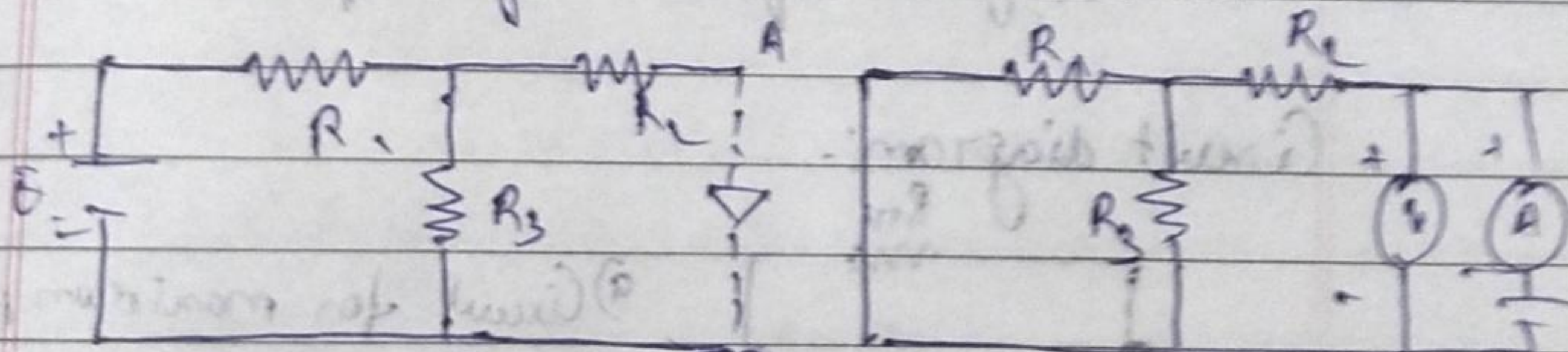

a) Norton Circuit Current circuit

b) Equivalent Resistor Circuit

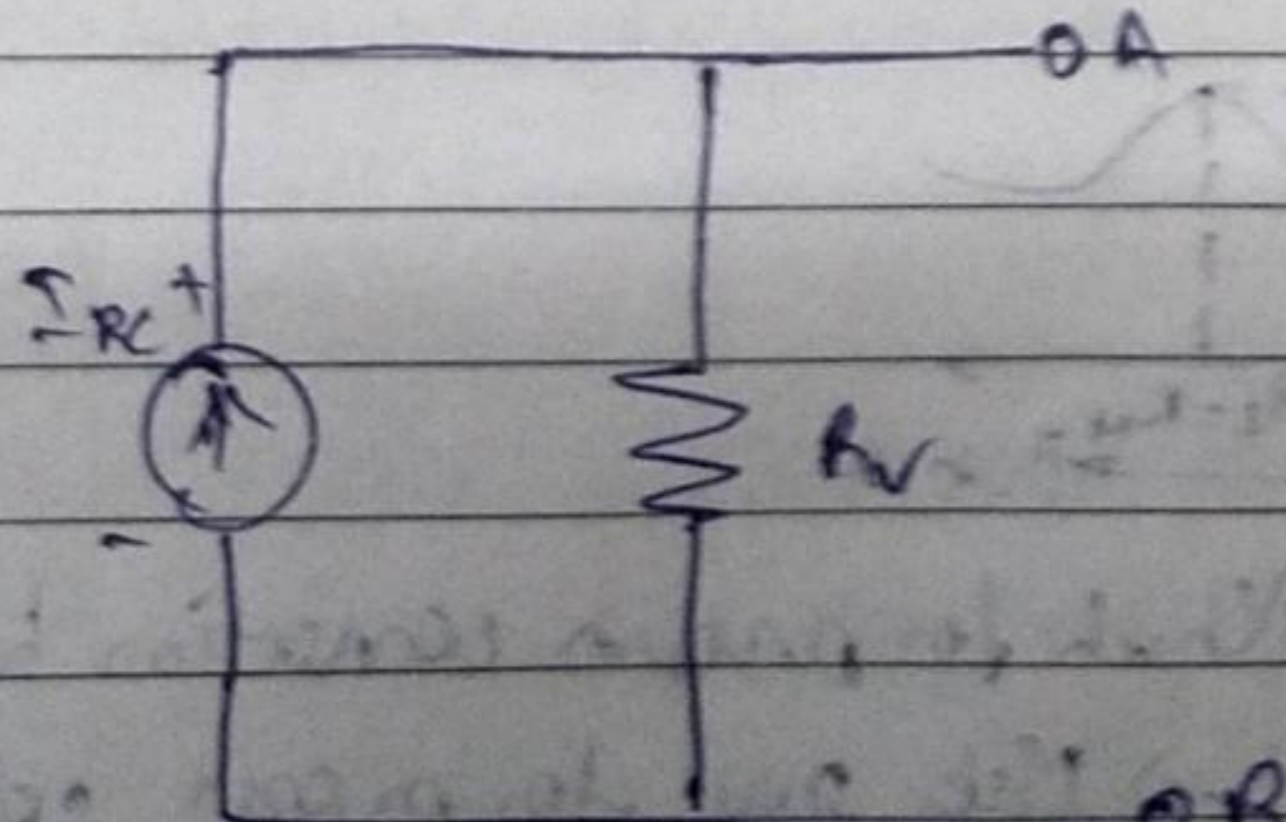


c) Norton equivalent

Procedure:- 1) Connect circuit diagram as shown
2) Measure V through A & B by short circuiting.
3) Connect circuit diagram shown in (B) and measure resistance R_V in A & B .
4) Draw Norton equivalent circuit by connecting I_N and R_N in parallel shown in (C)

d) Max Power Transfer Theorem


Statement:- The max power transfer theorem states that maximum power is load from a source to an load resistance when the load resistance is equal to source resistance, ($R_L = R_S$) is the condition required for maximum power transfer.

Circuit diagram:-

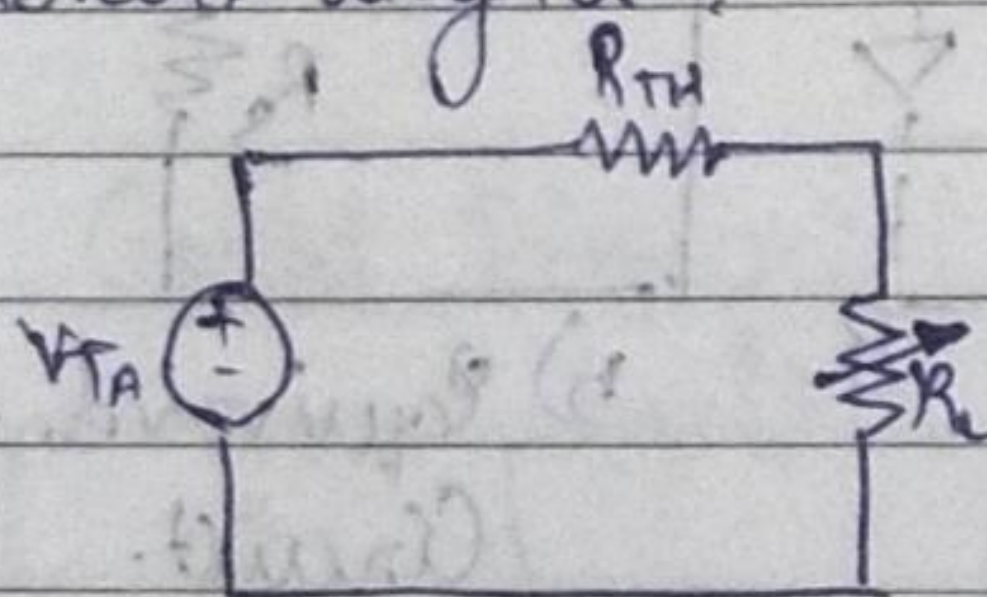

1) Circuit for maximum power transfer.

$$R_L = R_{TH}$$

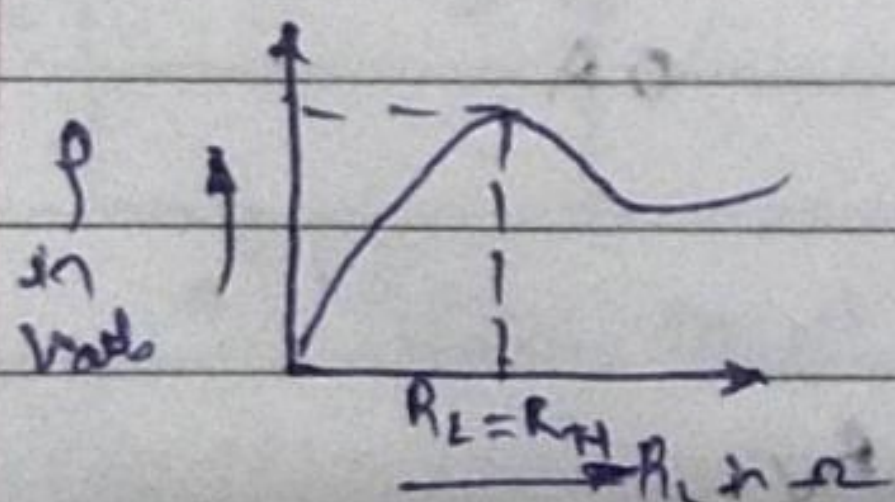

Precautions:- 1) Check for proper connection before switching on the supply. 2) Make sure for proper color resistor. 3) The terminal of the resistor shall be properly connected.
Conclusion:- We studied different network the for DC and AC circuit.