

Part B - Exp-2

Aim: To calculate and verify 'z' parameters of two port network.

Theory:- In 'z' parameter of two port, the input and output voltage V_1 and V_2 can be expressed in terms of output current I_1 and I_2 .

where V_1 and V_2 are dependent variable
 I_1 and I_2 are independent variable.


Thus,

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \dots (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \dots (2)$$

Here, Z_{11} and Z_{22} are inputs and output driving point impedance while Z_{12} and Z_{21} are reverse and forward transfer impedance.

Circuit diagram

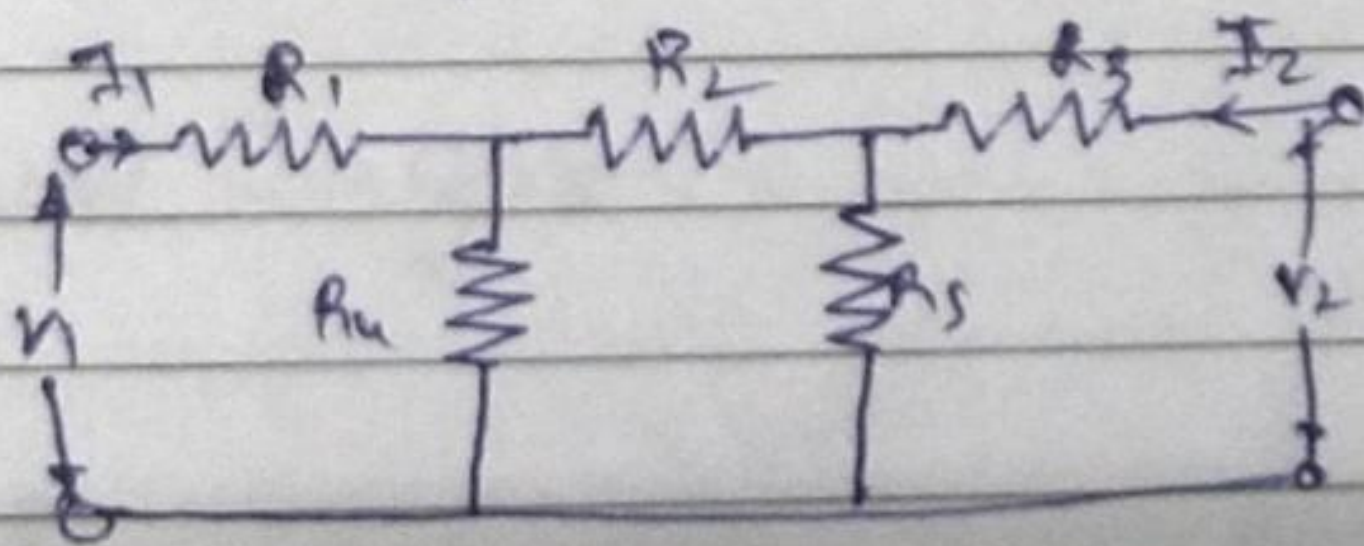

Procedure :-

- 1) Connect the circuit as shown in figure and switch on experiment board.

b) First, open the o/p terminal and supply 5V to i/p terminal. Measure o/p voltage & i/p current.

c) Second, open the i/p terminal and supply 5V to o/p terminal, measure i/p voltage and o/p current using multimeter.

d) Calculate the values of z-parameters using eqⁿ (i) and (ii).

e) Switch off the supply after noting down the readings.

Sample Calculation:-

i) When o/p is open i.e. $I_2 = 0$

$$Z_{11} = V_1 / I_1, \quad Z_{21} = V_2 / I_1$$

ii) When i/p is open i.e. $I_1 = 0$

$$Z_{12} = V_1 / I_2, \quad Z_{22} = V_2 / I_2$$

Conclusion:- The z-parameters of two port network has been verified.

