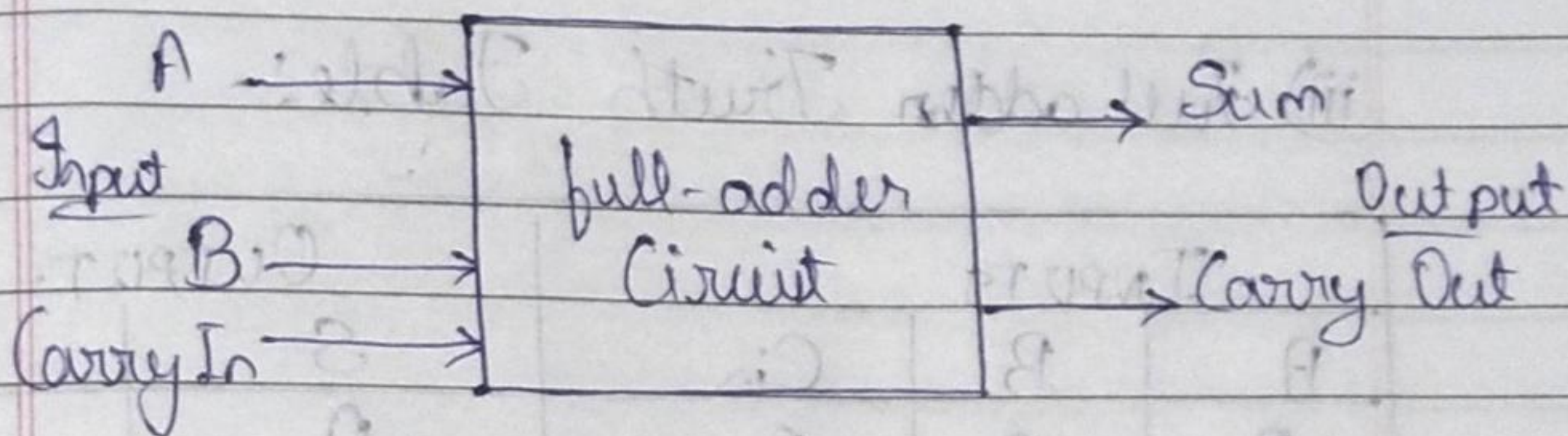


Part-A. Exp-3


Aim:- To study the about implementation of full adder circuit using gates.

Apparatus:- Bread board, connecting wires, IC 7408, IC 7486, IC 7432, IC 7400


Theory:- (i) A circuit called a full adder takes the carry-in value into account.



i) Full adder basic gates diagram:-

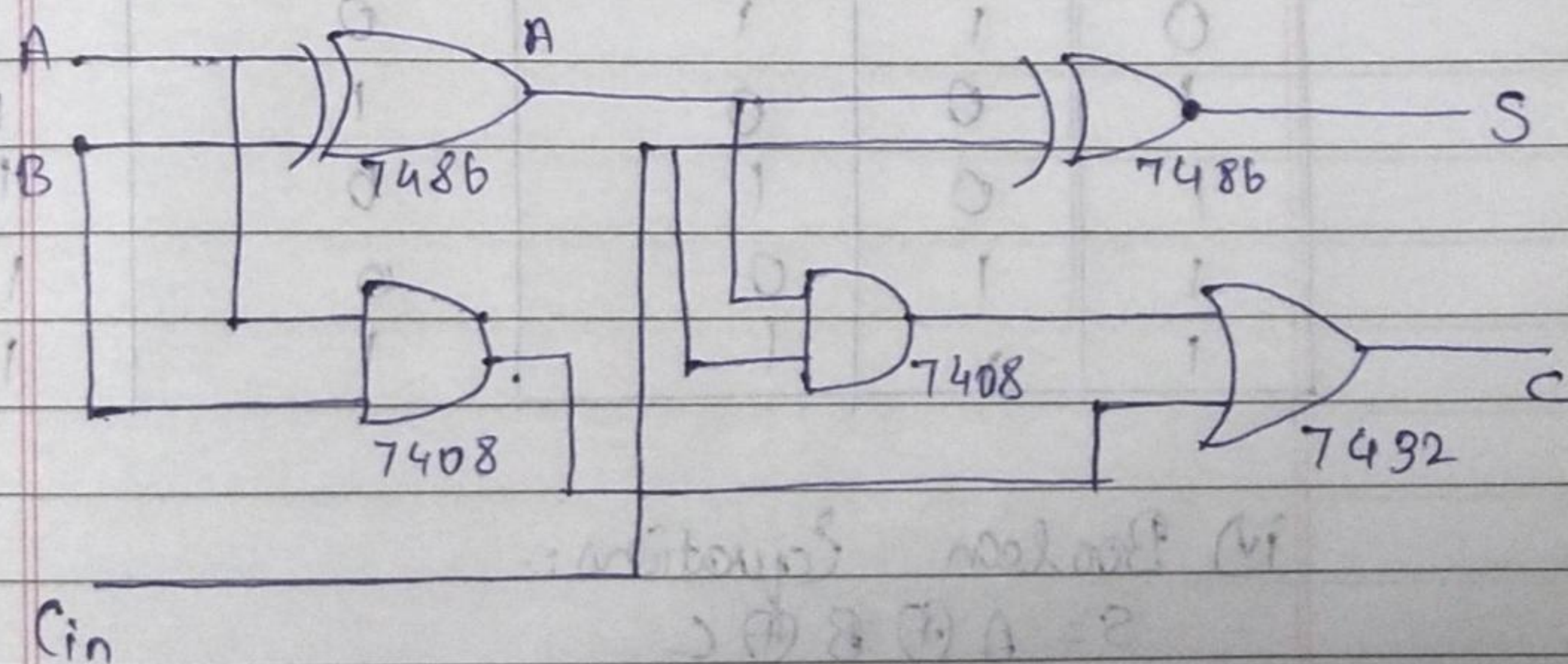

ii) NAND gate diagram:-

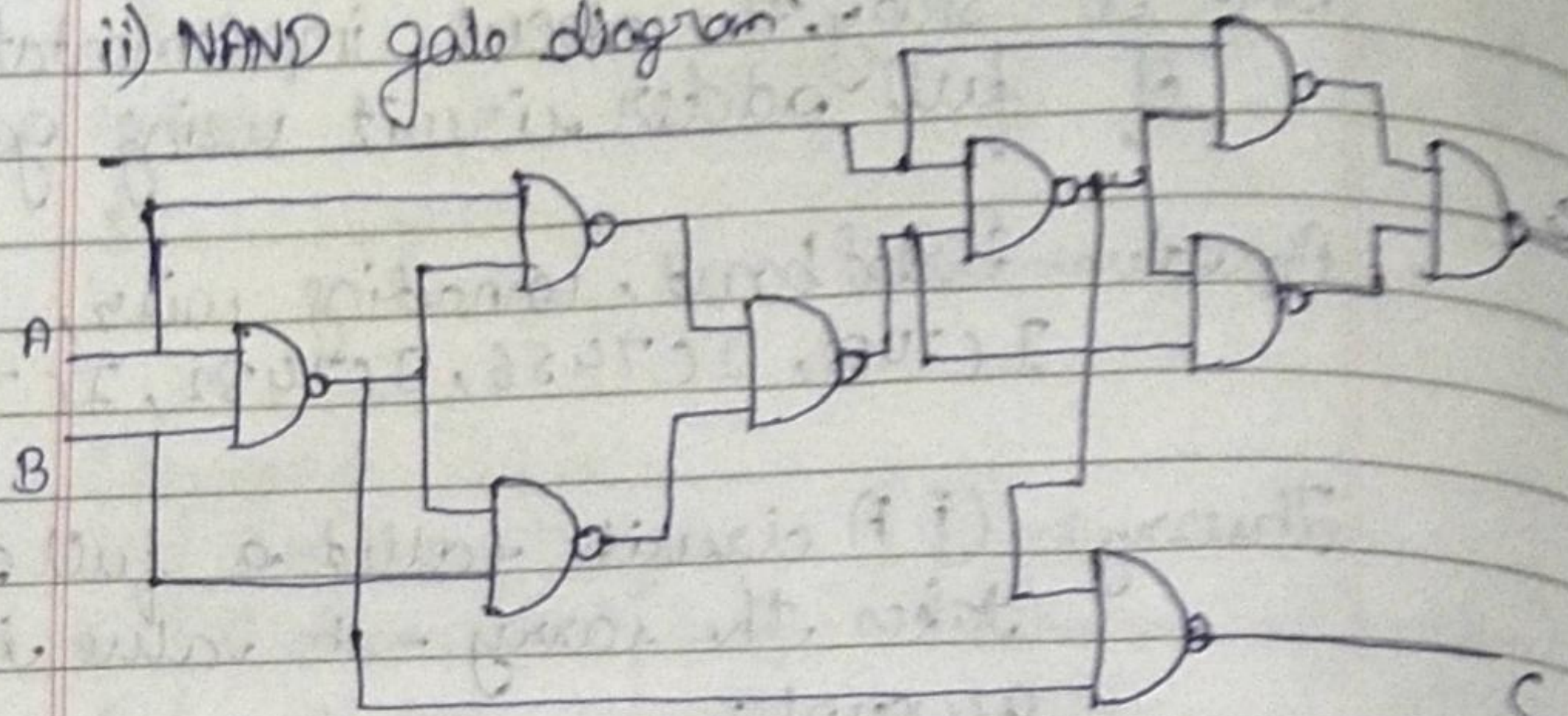

iii) Full adder Truth Table:-

INPUTS			OUTPUT	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

iv) Boolean Equations:-

$$S = A \oplus B \oplus C$$

$$C = AB + B C_{in} + A C_{in}$$

Conclusions:- Thus, we have studied about how a full adder circuit can be formed and implement and we also studied about that gates combinations can form different circuits. Which have different properties.